

EE314 Digital Electronics Laboratory

2017-2018 Spring Term Project Final Report

An FPGA Based Oscilloscope

1st Halil TEMURTAS 2094522 halil.temurtas@metu.edu.tr

2nd Erdem TUNA 2167419 erdem.tuna@metu.edu.tr

Abstract—The design of an FPGA based digital oscilloscope

Index Terms—FPGA, oscilloscope, ADC, VGA

I. INTRODUCTION

In this project, it is intended to realize a digital oscilloscope by using an FPGA. The FGPA will receive an analog signal, digitize it through an ADC; then will calculate the required parameters. Lastly data and input signal will be displayed on a VGA screen. The overall diagram is shown in *Figure 1*. The implementation logics and algorithms are discussed in respective sections.

 


Figure 1: The Block Diagram of the Project

II. ALTERA DE1-SoC

III. MODULES

The modules and functional blocks designed and used in the project are presented in this section.

A. ADC

This module quantizes the analog input data. The hardware used is LTC2308 that is built into the FPGA. The Altera provides an example code regarding the use of the built-in

 


Figure 2: The Block Diagram of the Project

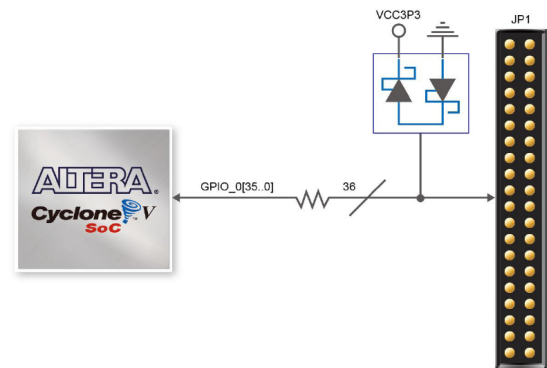


Figure 3: The Block Diagram of the Project

ADC[1]. By evaluating the provided functionalities of this example with the help of a MsC project [2], a code is written in Verilog HDL and in Qsys environment. Qsys instantiates the internal connections of embedded modules to use ADC controller. The resulting Qsys module is exported as BSF file and that is shown in *Figure 11*. This will be utilized as an ADC block. The code is written according to I/O ports of this block. But the ultimate ADC bus is output from "conduit_end_SDI" port of the ADC block.



Figure 4: The Block Diagram of the Project

 


Figure 5: The Block Diagram of the Project

 


Figure 6: The Block Diagram of the Project

B. RAM

The main function of RAM is to introduce a block to the system that can be both writable and readable. Writing is necessary to save data coming from ADC and reading is also necessary to process the data and show them on VGA

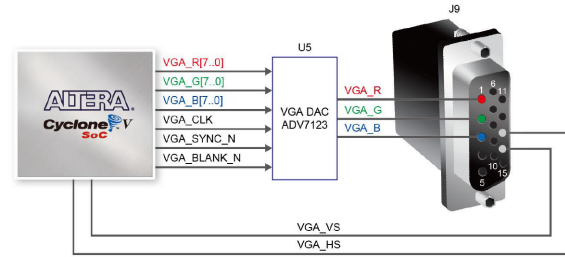


Figure 7: The Block Diagram of the Project

 


Figure 8: The Block Diagram of the Project

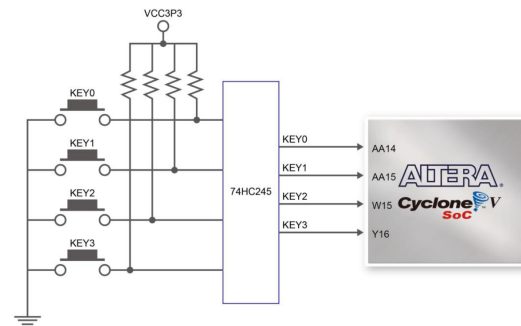


Figure 9: The Block Diagram of the Project

 


Figure 10: The Block Diagram of the Project

 


Figure 11: The Block Diagram of the ADC

 


Figure 12: FIFO Working Principle[3]

screen. The RAM should work with FIFO structure to realize proper operation on VGA screen. "A FIFO (first-in-first-out) buffer is an "elastic" storage between two subsystems." [3]. A FIFO based read and write operation is depicted in Figure 12. The RAM is designed in behaviour level however, yet not implemented. Possible state diagram for the RAM Module can be seen at Figure 13.

C. Computation Unit

Computation unit is the unit responsible for all kinds of mathematical calculation of the project. For instance mean value calculation for the input signal are conducted in this unit. This Unit can be considered as a brain of the project.

D. Mode Selection (AC/DC)

AC/DC Modes are one of the most fundamental mods of digital oscilloscopes in market. In this part we will build a module to build our own selection mode. One slide switch will be assigned to retrieve the desired mode information from the user. Based on this information, screen will display the input signal either with the DC offset or without the DC offset.

1) *AC Mode:* In AC Mode operation of the oscilloscope, the DC offset voltage is removed from the input voltage before it is reflected to the VGA monitor. For that Computation Unit will be used to extract offset information from stored data.

 


Figure 13: State Diagram for RAM

2) *DC Mode:* In DC Mode operation of the oscilloscope, the DC offset voltage is untouched from the stored data of the input voltage. The stored data is reflected directly to the VGA monitor.

E. VGA Screen

VGA is a widely used standard in video industry for the transmission of video signals from a computer or microprocessor into a monitor or TV. Each 640x480 image is called a 'frame' and each frame contains 480 lines which are made up of 640 pixels. We will use a standard LCD VGA Monitor as a display for our FPGA Oscilloscope. We will build a controller module for this part called VGA Controller. The input pin configuration for the VGA Monitor can be seen at Figure 14.

 


Figure 14: VGA Input Pins

1) VGA Controller:

The VGA controller combines the data from RAM and Computation Unit to create a signal that can be displayed on the VGA monitor. Each of the RAM Modules contains an image that is ready for display on the screen. However, the data must be positioned relative to each other and combined. Also this module performs once a second as desired in the project requirements. The VGA controller also gets data from

different data inputs such as Time/div and Voltage/div in order to reflect the waveform as user requires. In this part multiple clock signals and counters needed to display the waveform accordingly. Basic VGA Controller can be seen at Figure 15[4].

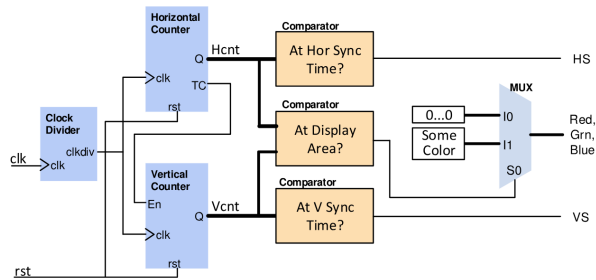


Figure 15: VGA Controller

This module will supply an input data for the VGA controller for user preferences. Two push buttons will be assigned for the Time/div inputs that can be considered as Time+/div and Time-/div. As user pushes to Time+/div button, the time scale will be larger than the previous value. Similarly, as the user pushes to Time-/div button, the time scale will be smaller than the previous value. According to user preferences, this module allows user to see wider or narrower parts of input waveform.

2) Voltage/div Input:

This module will supply an input data for the VGA controller for user preferences. Two push buttons will be assigned for the Voltage/div inputs that can be considered as Voltage+/div and Voltage-/div. As user pushes to Voltage+/div button, the voltage scale will be larger than the previous value. Similarly, as the user pushes to Voltage-/div button, the voltage scale will be smaller than the previous value. According to user preferences, this module allows user to fit the voltage waveform to the screen.

3) Autoscale Input:

This module will also supply an input data for the VGA controller for user preferences. Since we are planning to use all push buttons for other modules. One slide switch will be assigned to this module. As the user triggers the button, this module will scale the waveform for the display such that it fits the display best.

IV. CONCLUSION

In this project, our aim is to design a FPGA based digital oscilloscope using Verilog. The project consists of five main part that are Analog to Digital Converter (VGA), RAM, Computation Unit, Mode Selection for Display and VGA Screen. Overall diagram of the project can be seen at Figure 1.

REFERENCES

- [1] "De1-Soc CD." [Online]. Available: http://download.terasic.com/downloads/cd-rom/de1-soc/DE1-SoC_v.5.0.1_HWrevF_SystemCD.zip. [Accessed: 21-May-2018].
- [2] "Digital Scope Implemented on Altera DE1-SoC." [Online]. Available: https://people.ece.cornell.edu/land/courses/eceprojectsland/STUDENTPROJ/2015to2016/hj424/hj424_report_201605191237.pdf. [Accessed: 21-May-2018].
- [3] P.P. Chu, Embedded SoPC Design with NIOS II Processor and Verilog Examples. New Jersey, 2012.
- [4] "VGA Display Controller" [Online]. Available : <https://learn.digilentinc.com/Documents/269>